



Hajee Mohammad Danesh Science and Technology University, Dinajpur

Department of Computer Science and Engineering

B. Sc. in Computer Science and Engineering

Semester Final Examination 2017 (Jul-Dec)

Level 4 Semester II, Course Code: CSE 457, Credit: 3.0

Course Title: VLSI Design

Time: 03 Hours

Total Marks: 90

[N.B. The figure in the right margin indicates the marks allocated for respective question. Split answer of any question will not be accepted.]

SECTION-A

(Answer any three from the following questions.)

1. (a) Describe VLSI IC family. Briefly explain the other IC families with an example for each. 2+3
- (b) Explain the speed/performance scenario of nMOS, CMOS, GaAs, BiCMOS, and ECL technologies. 5
- (c) Define bipolar transistor technology. Explain different types of MOSFET briefly. 2+3
2. (a) What is MOS and why it is important in VLSI? 1+2
- (b) State the guidelines to design a VLSI system. Discuss different types of symbols used in stick diagram. 2+3
- (c) What is fabrication in context of transistor technology? Briefly discuss about nMOS fabrication. 1+6
3. (a) Explain pass transistor and switch logic for VLSI design. 1+2
- (b) Compare between unipolar and bipolar transistor technology. 5
- (c) Derive the drain to source current I_{ds} versus voltage V_{ds} relationship equations for the non-saturated region as well as the saturated region. 7
4. (a) Define analog and digital IC. 3
- (b) Deduce the pull-down ratio $Z_{p.u.}/Z_{p.d.}$ for an inverter driven by another nMOS inverter. 5
- (c) Shortly describe the operational procedure of a multiplexer and design it through stick diagram using pass transistor switch logic. 7

SECTION-B

(Answer any three from the following questions.)

1. (a) Explain CMOS stick diagram design style with an example. 5
(b) What is transmission gate? Discuss regularity factor of a VLSI design with an example. 2+3
(c) Draw the basic circuit of BiCMOS inverter and describe its operating principle. 3+2
2. (a) Mention the necessities of transistors in VLSI design. Write short note on Lambda based design rules for stick diagram. 2+3
(b) Discuss the operational procedure of a typical parity generator and draw its stick diagram. 2+3
(c) Define a full adder. Draw its stick diagram using multiplexer based switch logic. 2+3
3. (a) Show and briefly illustrate the stick diagram (outline) of a 4-bit adder. 5
(b) Discuss the bus arbitration logic for n -line bus in favor of VLSI design. 5
(c) Explain the subsystems of a typical ALU. 5
4. (a) How can a 4-bit adder be used for implementing the logical operations of a 4-bit ALU? Explain with proper Boolean expressions. 5
(b) Discuss the operational procedure of a 2-input AND gate and design it through logic diagram, transistor circuit diagram and stick diagram. 5
(c) Draw and discuss the stick diagram (outline) of a 4-bit ALU. 5